

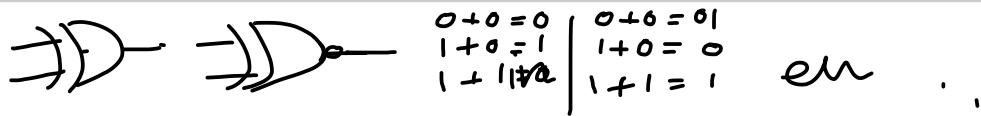
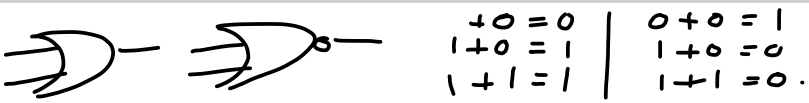


Gates →

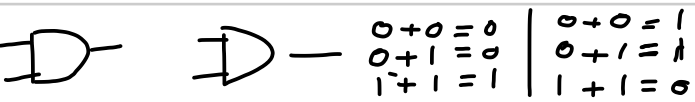

$$F = abc + a\bar{b}c + d.$$

↳ draw this circuit

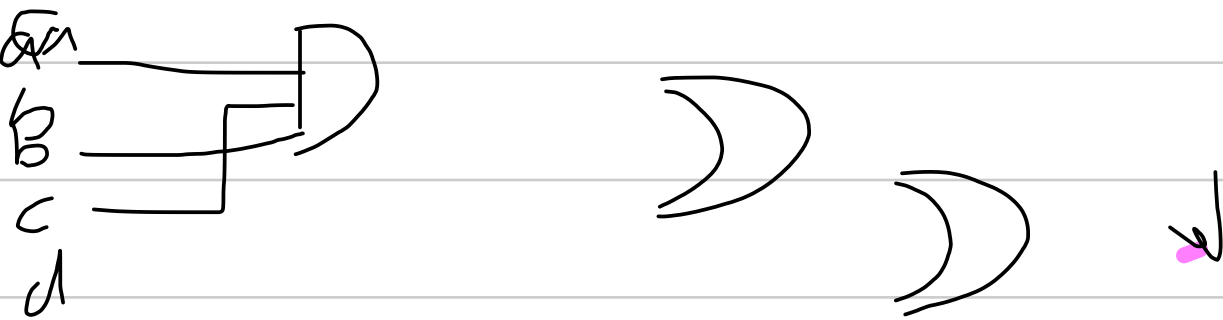


$$f = abc + a\bar{b}c + d$$


Definitions are important here !!

$$f = ac + d$$


2-port gates

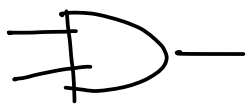

3-port gates.

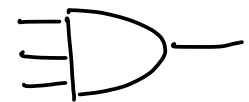

Unlimited

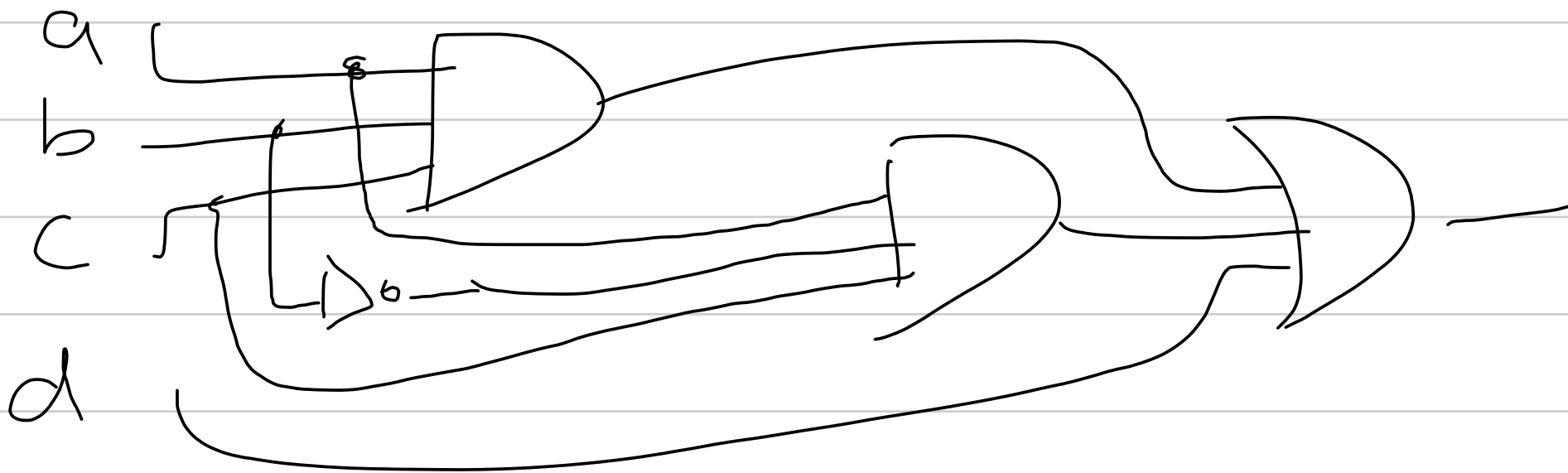



17 AUGUST 2011

MUXs & DeMUXs - recap

Gated circuits

Block diagrams \rightarrow black box


Decoders & Encoders.

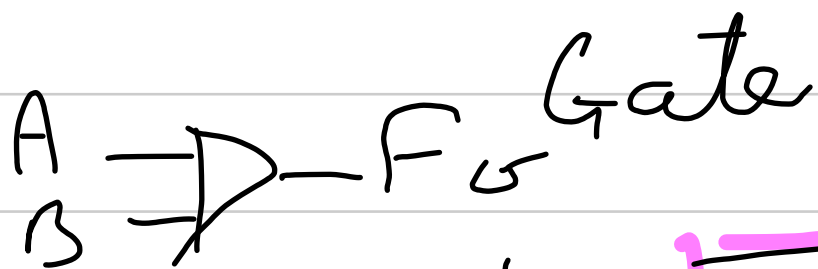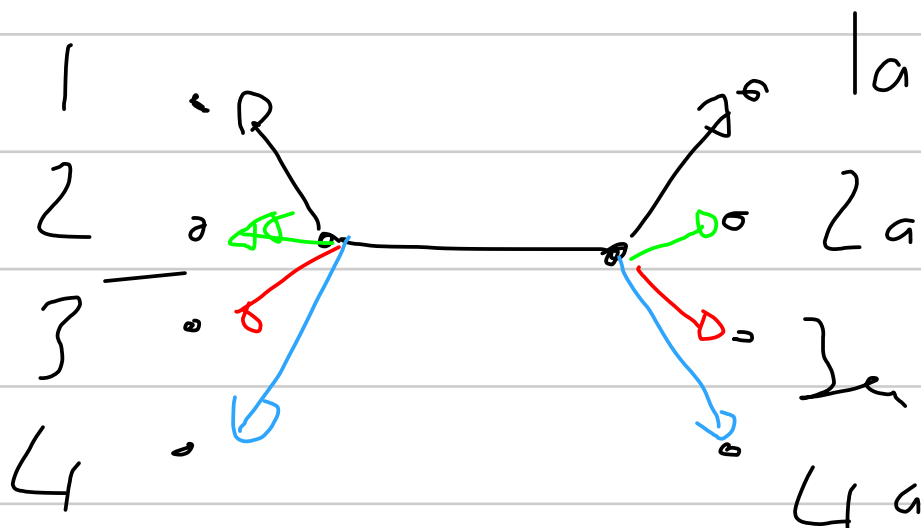

Block



DECODERS

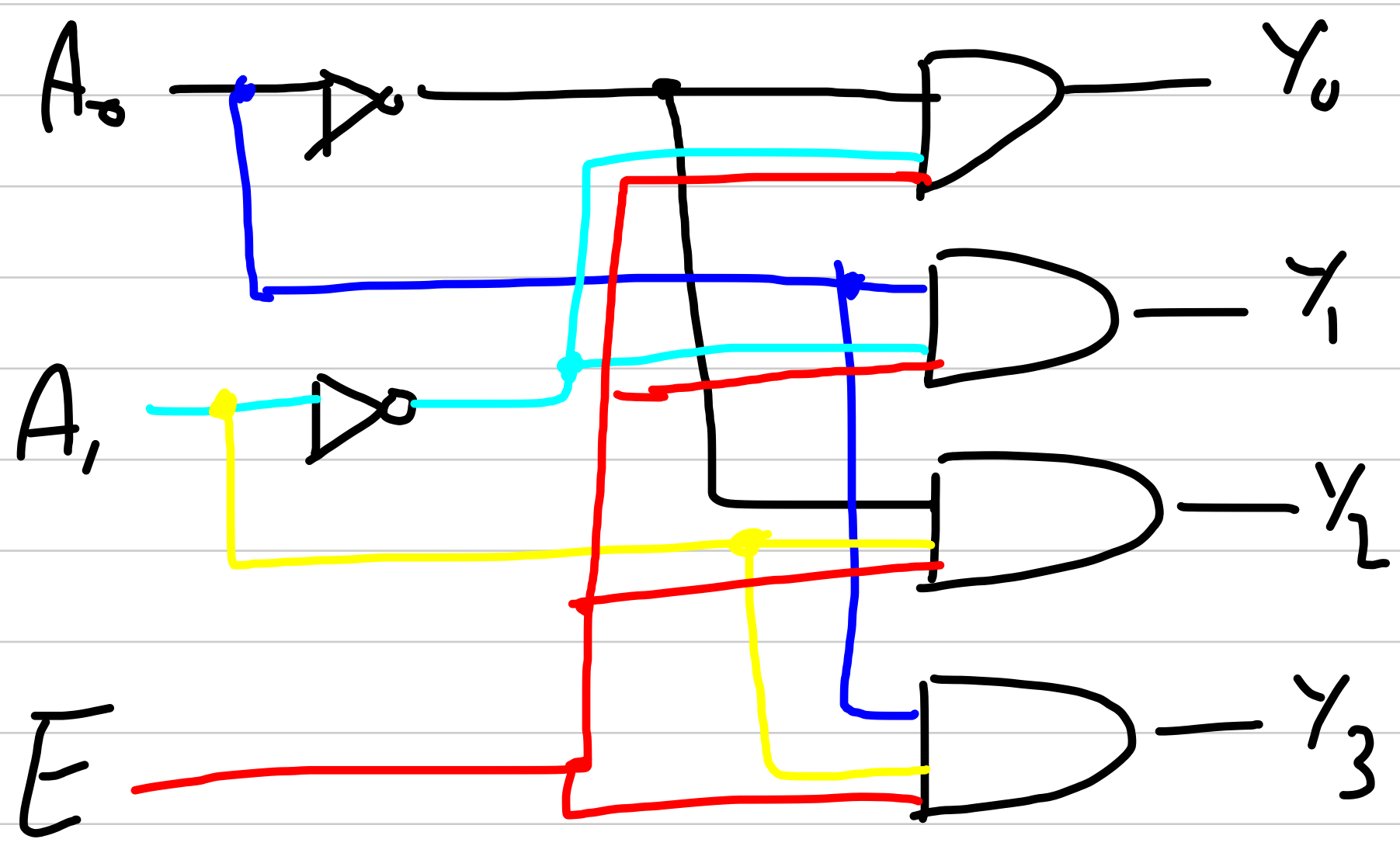

TRUTH TABLE

E A₀ A₁ Y₀ Y₁ Y₂ Y₃


0 X X 0 0 0 0

1 0 0 1 0 0 0

1 1 0 0 0 1 0 0

1 0 0 1 0 0 1 0


1 1 1 0 0 0 1

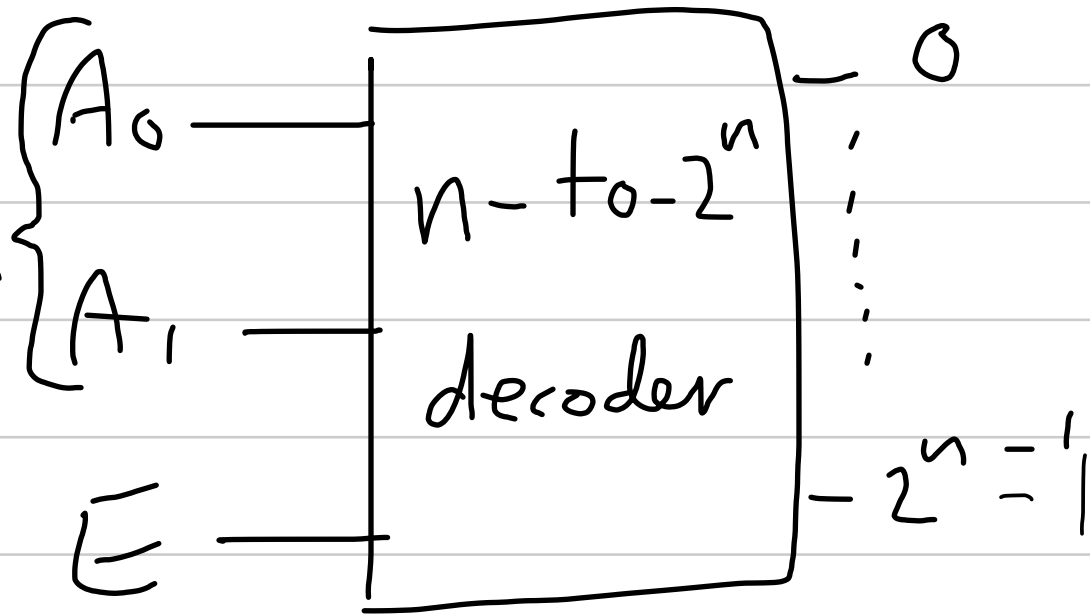


$n = 2$

$2^n = 4 = m.$


2 to 4 bit decoder

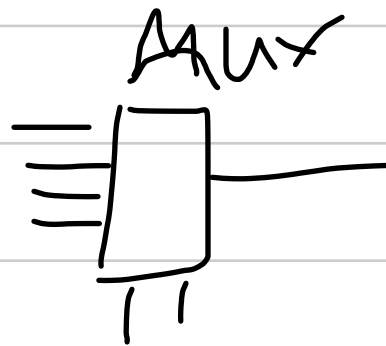

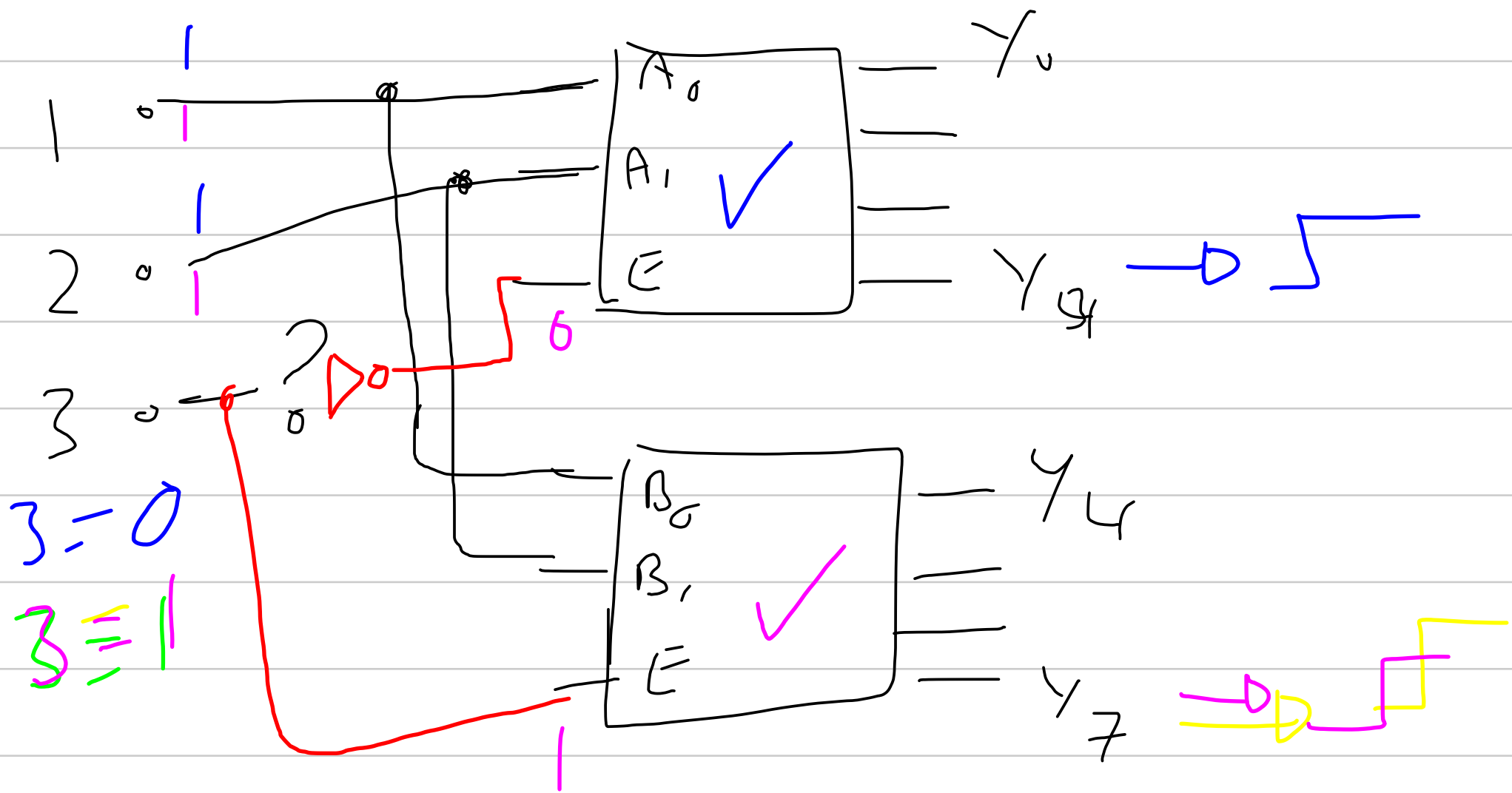3 to 8 decoder using 2 to 2 to 4 bit decoders



Encoders.

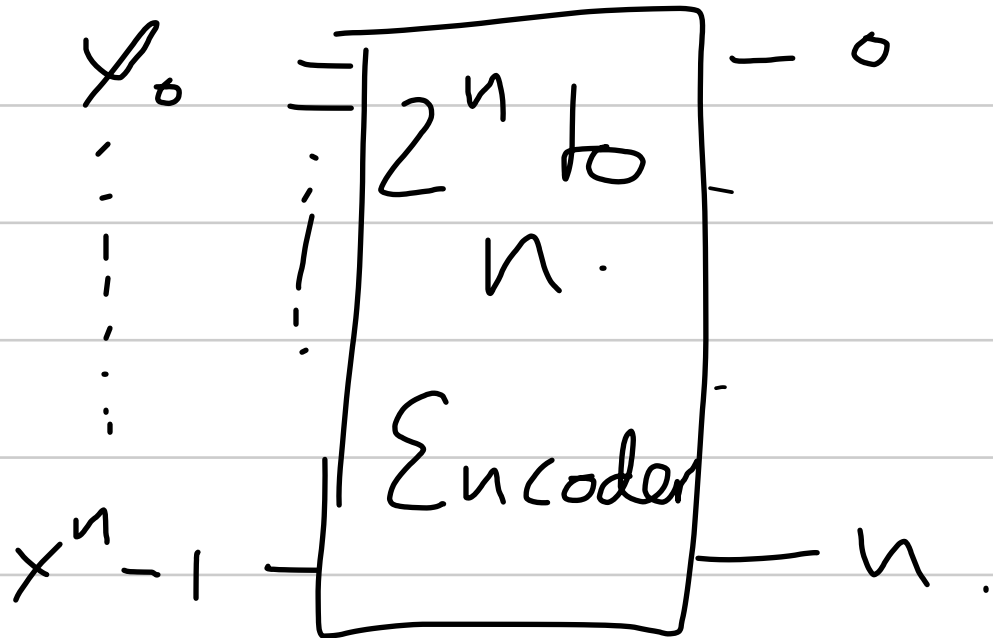

X_0	X_1	X_2	X_3	X_4	X_5	X_6	X_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	_____				0	0	1	
0	0	1	0	_____			0	1	0	
0	0	0	1	0	_____		0	1	1	
0	_____		0	1	0	0	0	1	0	0
0	_____			0	1	0	0	1	0	1
0	_____				0	1	0	1	1	0
0	_____					0	1	1	1	1

Priority
descent