

Microprocessors


Andrew Dickson

Andrew.dickson@wits.ac.za




University of the Witwatersrand, Johannesburg

Basic building blocks - Gates

 


Inverter

$1 * 0$
 $0 * 1$

 


AND

 $0 + 0 = 0$
 $0 + 1 = 0$
 $1 + 0 = 0$
 $1 + 1 = 1$




NAND

 $0 + 0 = 0$
 $0 + 1 = 1$
 $1 + 0 = 1$
 $1 + 1 = 0$



OR

 $0 + 0 = 0$
 $0 + 1 = 1$
 $1 + 0 = 1$
 $1 + 1 = 1$




NOR

$0 + 0 = 1$
 $0 + 1 = 0$
 $1 + 0 = 0$
 $1 + 1 = 0$



XOR

 $0 + 0 = 0$
 $0 + 1 = 1$
 $1 + 0 = 1$
 $1 + 1 = 0$



XNOR

$0 + 0 = 1$
 $0 + 1 = 0$
 $1 + 0 = 0$
 $1 + 1 = 1$

Boolean simplification

$$Q = \bar{A}\bar{B}C + \bar{A}BC + ABC$$

$$Q = \bar{A}C(\bar{B} + B) + BC(\bar{A} + A)$$

$$Q = \bar{A}C + BC$$

$$Q = C(\bar{A} + B)$$

$$Q = \bar{A}C(\bar{B} + B) + ABC$$





$$Q = \bar{A}C + ABC$$

$$Q = C(\bar{A} + AB)$$

$$Q = C(\bar{A} + B)$$




Karnaugh maps

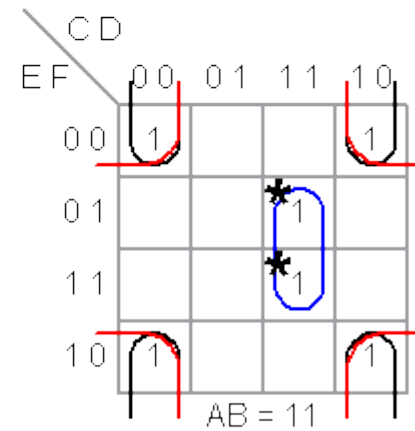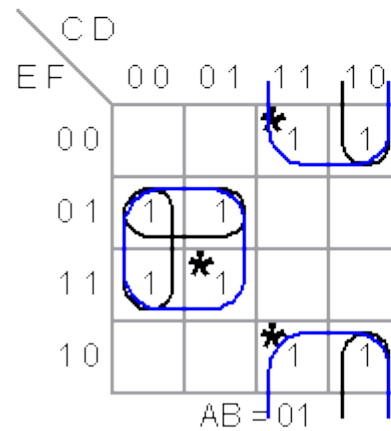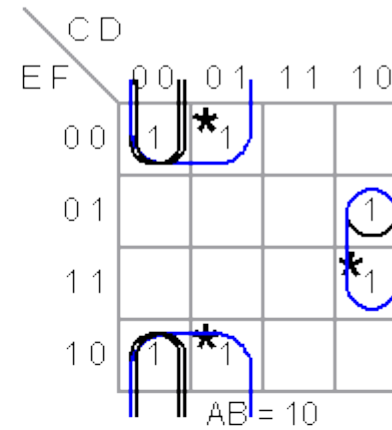 


Definitions

➤ **TTL, CMOS**

➤ **Gated Diagram –**

 

➤ **Block diagram –**

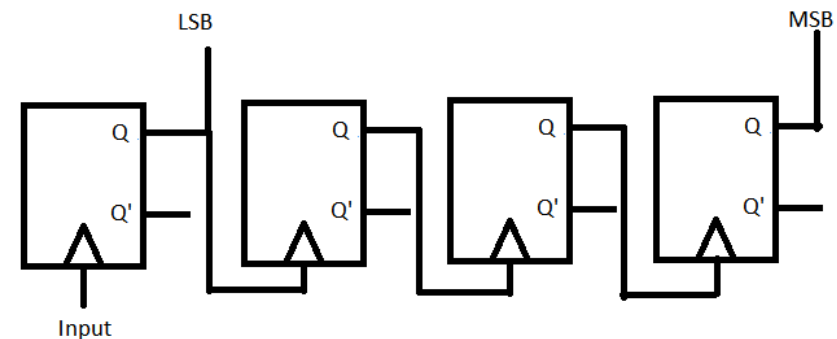


➤ **Combinational logic**

➤ **Sequential logic**


Decoders

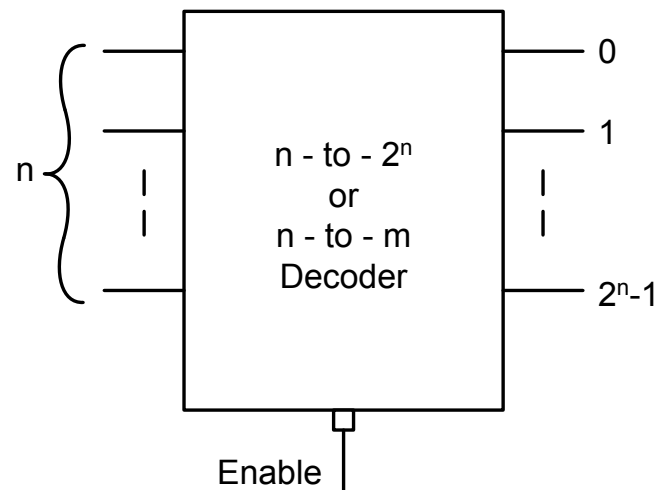- Device that decodes an input
- Multiple input multiple output device
- n inputs $\rightarrow 2^n$ outputs
- $2^n = m$ where the device is called **n-to-m decoder**




Decoder cont.

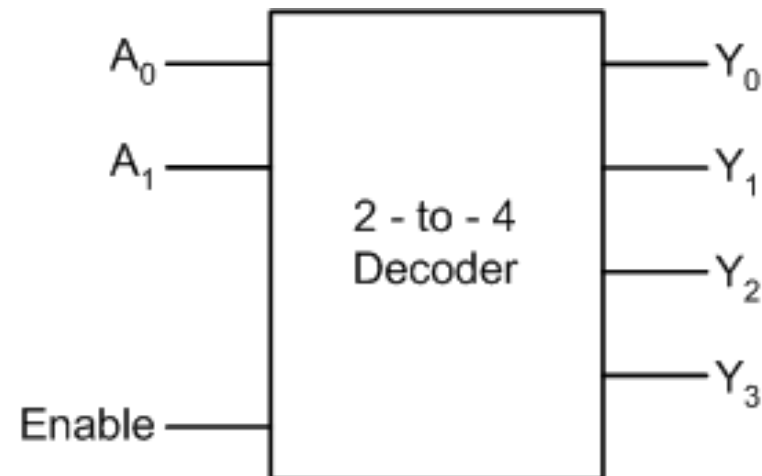- A decoder activates exactly one of its outputs based on the input values
- Example – 2 – 4 bit decoder




Decoder cont.

 

Decoder cont.


A_0	A_1	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
1	0	0	1	0	0
0	1	0	0	1	0
1	1	0	0	0	1

Decoders cont.

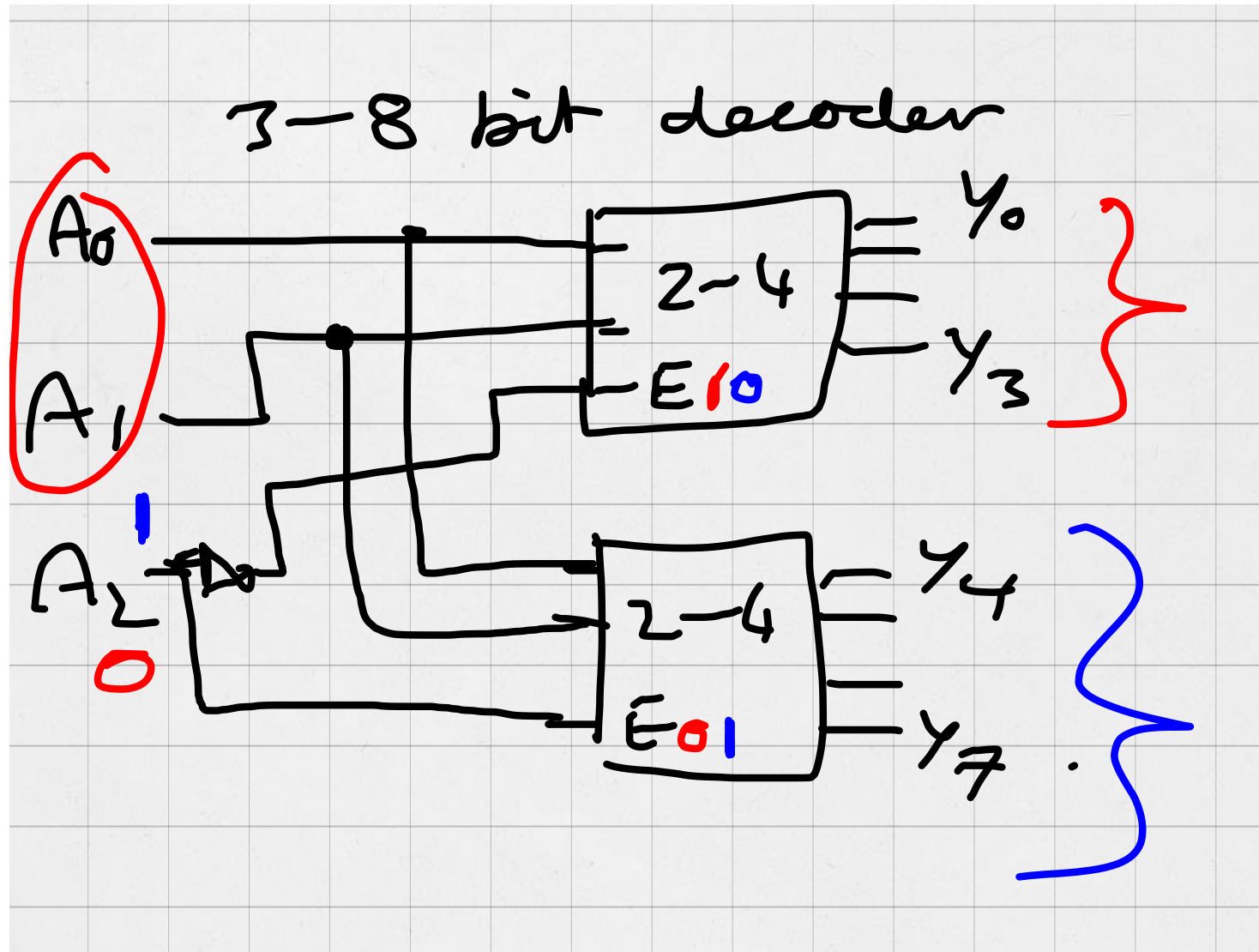

Encoder

 - Inverse of a decoder
- 2^n inputs \rightarrow n outputs
- Only 1 active high input



Encoders cont

X_0	X_1	X_2	X_3	X_4	X_5	X_6	X_7	Y_2	Y_1	Y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

