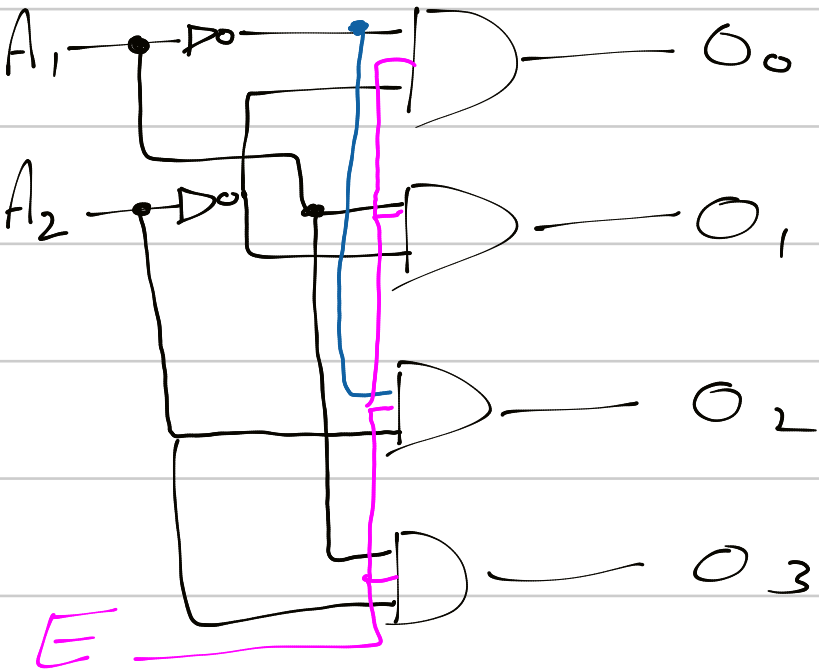


Andrew Dickson


Andrew.dickson@wits.ac.za

ELEN2006 - digital logic

Decoders:



A_1	A_2	O_0	O_1	O_2	O_3
0	0	1	0	0	0
1	0	0	1	0	0
0	1	0	0	1	0
1	1	0	0	0	1

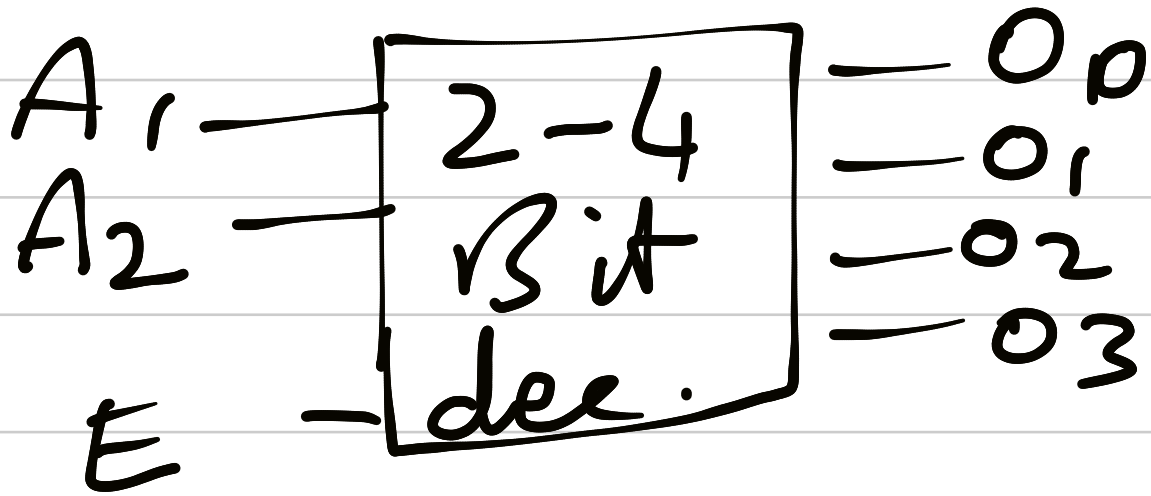

3-8 Bit Decoder - Block diagram

