 


29 August 2013



Recap: Sequential Logic

- edge and level triggering
- latches vs flip-flops
- SR, JK, Master slave, D
- Timing/ triggering diagram



Must use NOR gates, if you use OR gates the latch will not work!

# Ripple counter, or frequency divider!

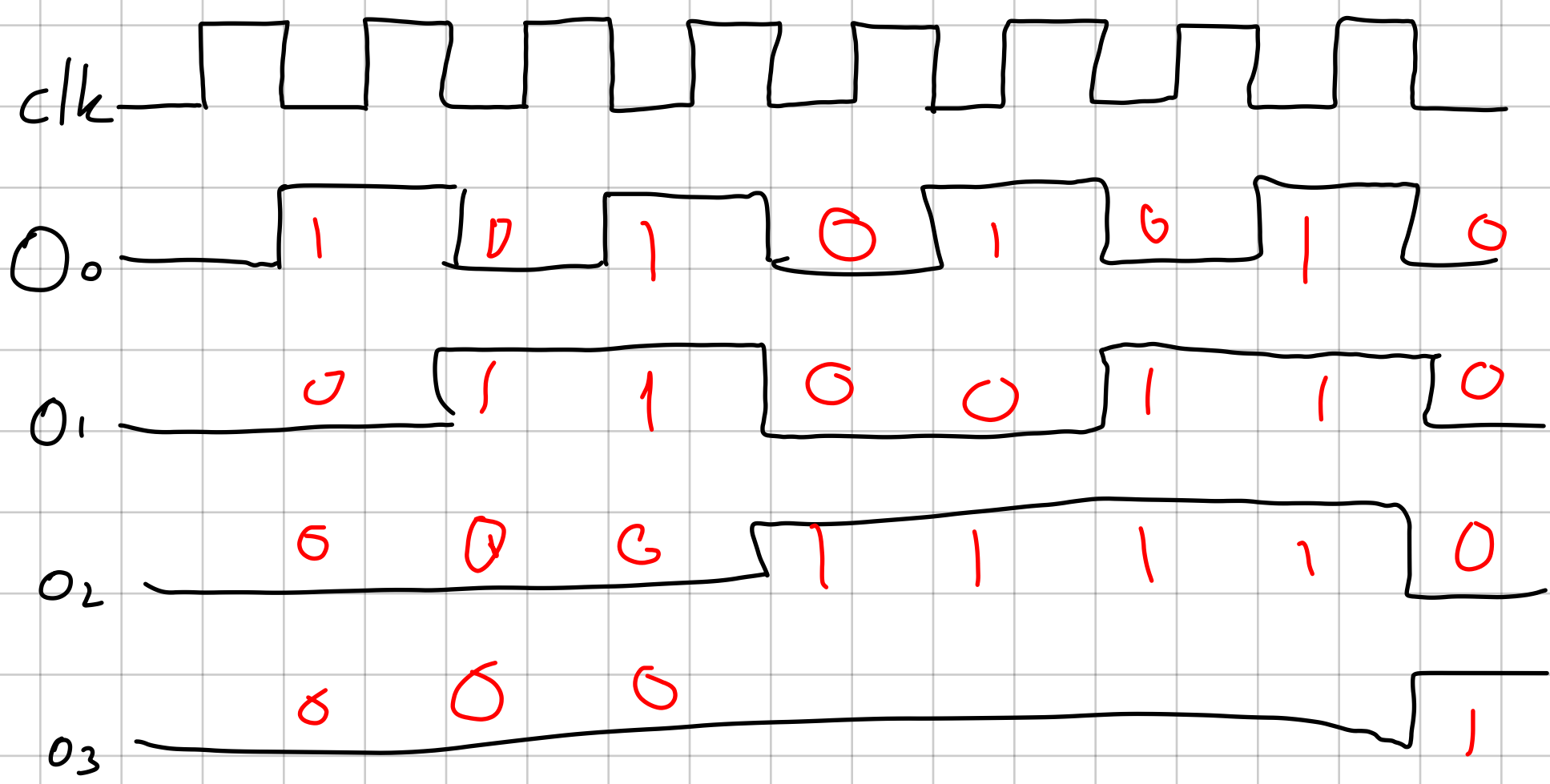 

Discussed the test process/solutions, with particular reference to question 4, HV test station