

Test

(Closed-book; One double-sided A4 formula sheet allowed.)

Time: 80 minutes

Total: 30

Date: 8 September 2010

Question 1 [10 marks]

Use block diagram algebra to derive the overall transfer function for the system in Figure 1.
Important: Marks will only be awarded if the quotients are simplified as far as possible.

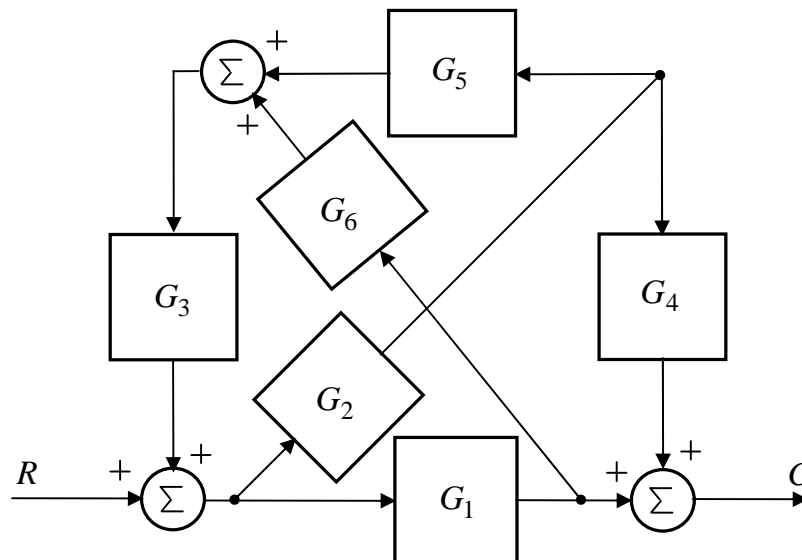


Figure 1. Block diagram of a complex system.

Question 2 [20 marks]

For small-signal analysis the circuit of a phase-shift oscillator effectively reduces to that shown in Figure 2(a). (The assumptions here are that the effective resistance of the biasing network is significantly greater than the value of R and that all bypass capacitors, blocking capacitors and coupling capacitors are effectively short circuits at the frequency of interest.) With the small-signal analysis model of a

bipolar junction transistor shown in Figure 2(b) the phase-shift oscillator's circuit reduces to that shown in Figure 2(c). An additional simplifying assumption made here is that each of the resistances of the phase-shift network and the transistor's base-emitter junction resistance are all equal as are the capacitors in the phase-shift network.

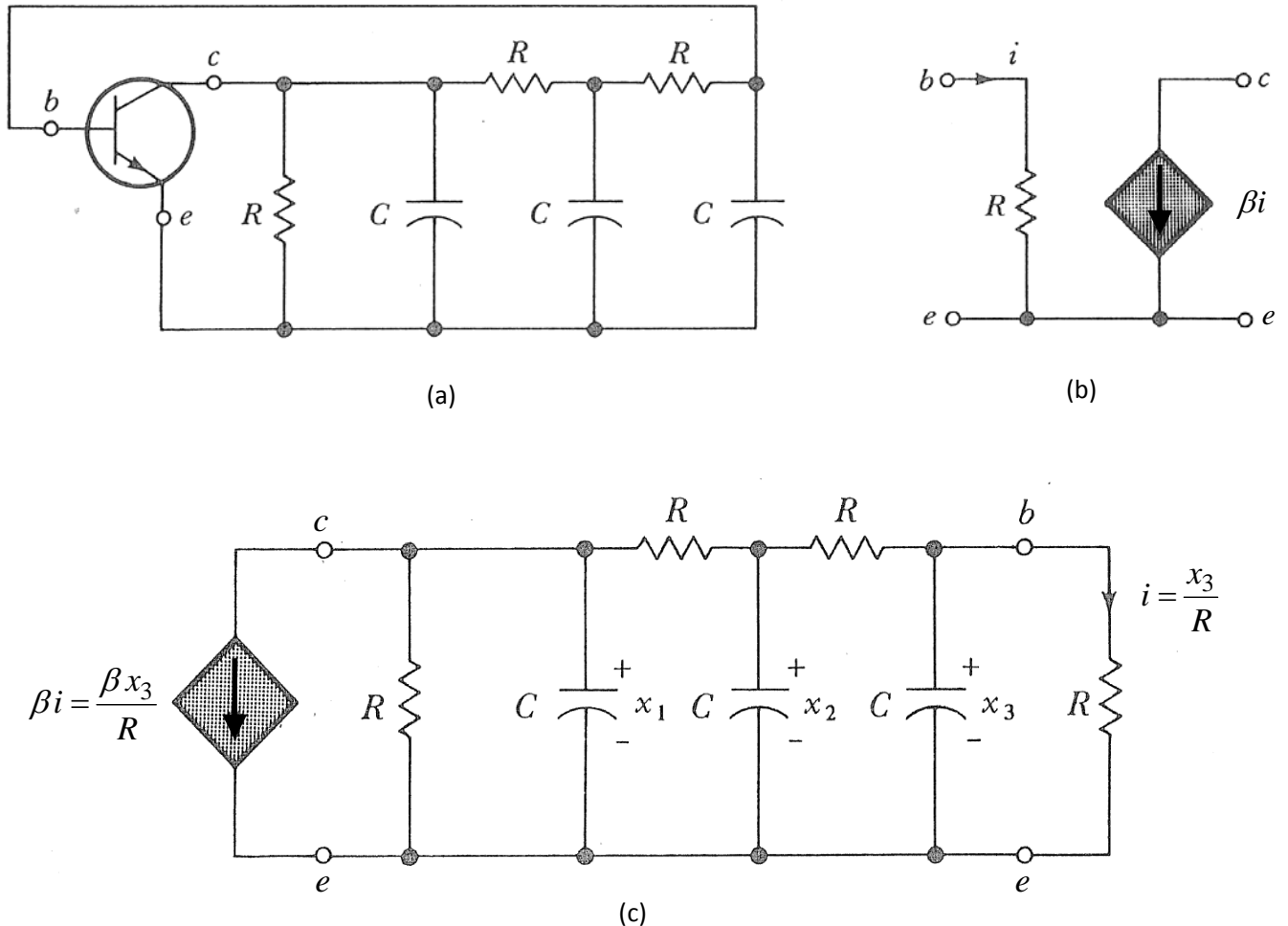


Figure 2. Phase-shift oscillator.

- Derive the dynamical equation for the phase-shift oscillator.
- From the dynamical equation determine the parameter values β and $a = 1/RC$ for which the circuit will oscillate as well as the frequency at which it will oscillate.

Hints:

- Choose the voltages across the capacitors as state variables (as indicated in Figure 2(c)) to obtain the state space representation for this circuit.
- Next, derive the system's characteristic equation namely $s^3 + 6as^2 + 10a^2s + (\beta + 4)a^3 = 0$ and then use the Routh-Hurwitz stability criterion for determining the conditions for which the circuit will oscillate.